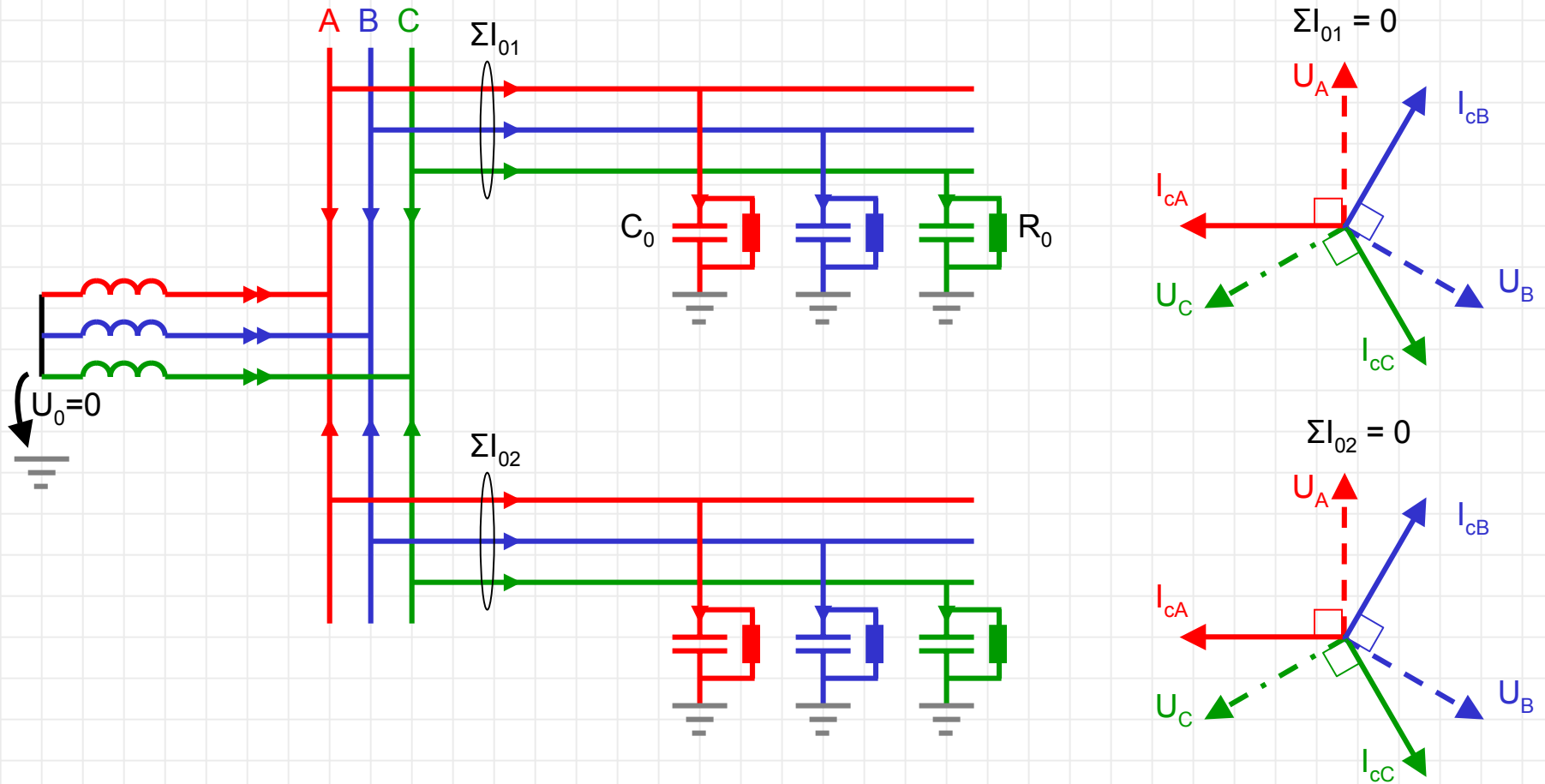


# Unfaulted unearthed network




- Phase-to-ground voltages form a symmetrical system and their sum equal to zero at every time instance
- Capacitive charging currents ( $I_{cA}$ ,  $I_{cB}$ ,  $I_{cC}$ ) flow through the phase-to-earth capacitances and form a symmetrical system
- $I_0$  measurement in feeder #1 ( $\Sigma I_{01}$ ) measures the sum of the charging currents of that feeder, which equals to zero
- $I_0$  measurement in feeder #2 ( $\Sigma I_{02}$ ) measures the sum of the charging currents of that feeder, which equals to zero

# Single phase to earth fault in unearthed network

## Single-phase to earth fault in phase C


### Equivalent circuit

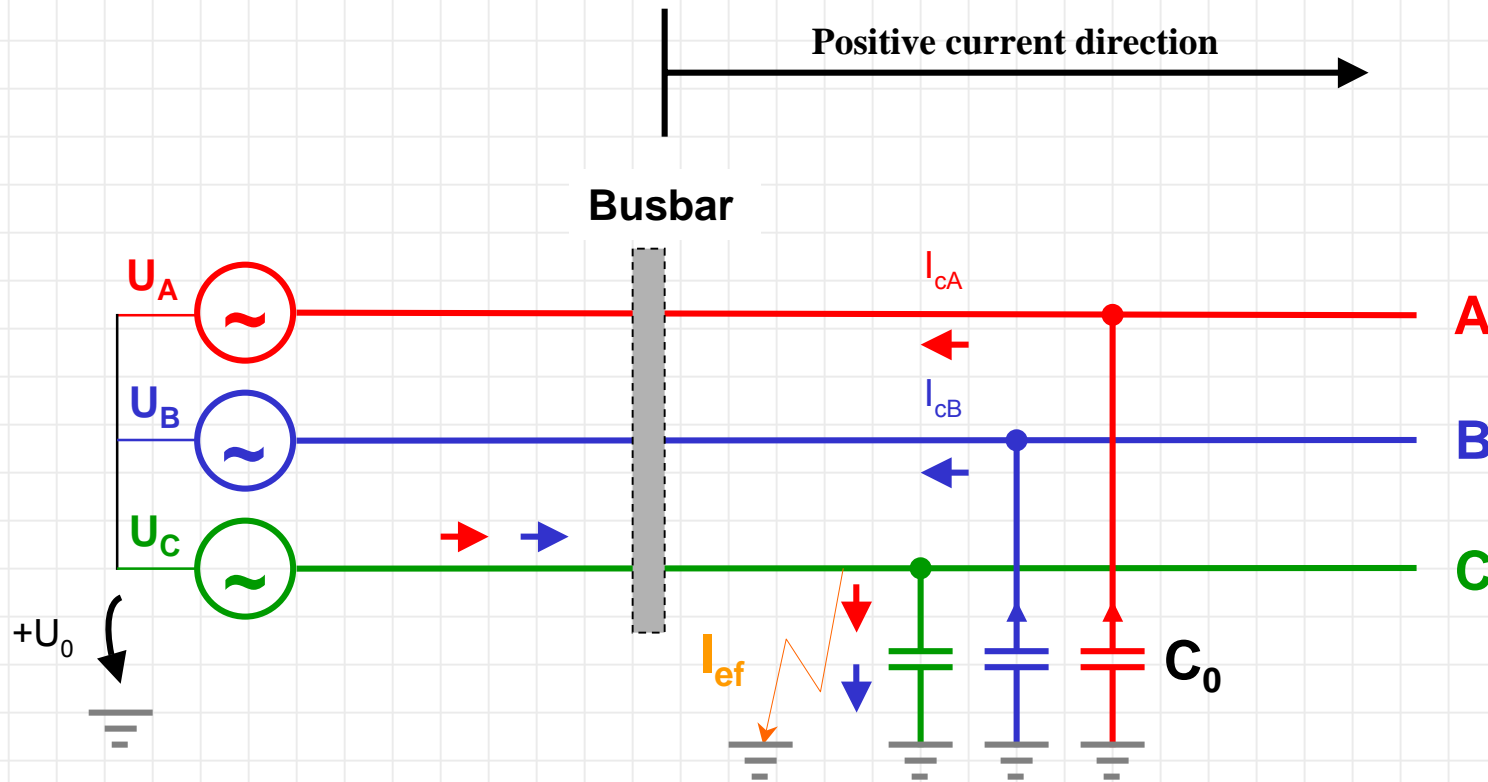


- In healthy phases charging current flows **towards the busbar**
- In faulty phase the earth fault current (sum of charging currents of the healthy phases) flows **towards the fault location**
- **Positive current direction is selected to be from busbar to feeders**
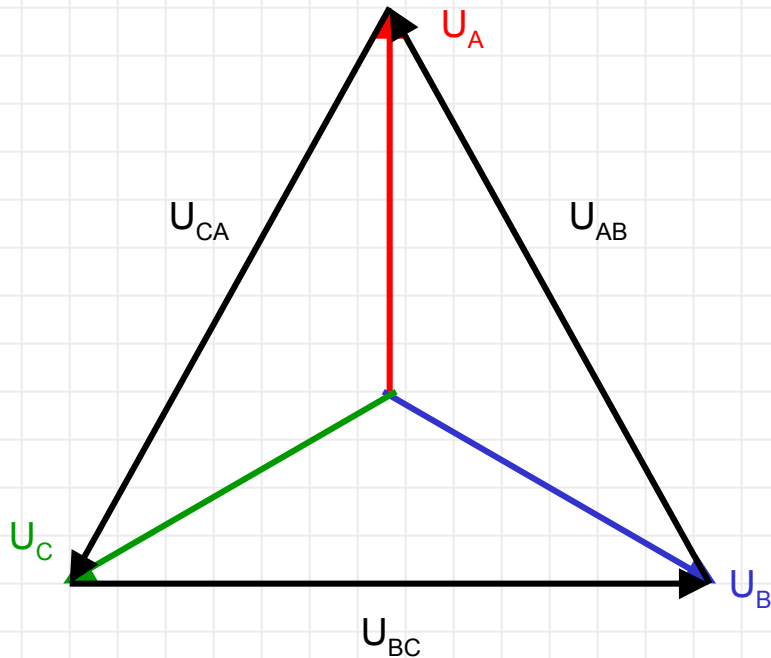
# Single phase to earth fault in unearthed network

Single-phase to earth fault in phase C - What happens to voltages?



Voltage phasors before the fault

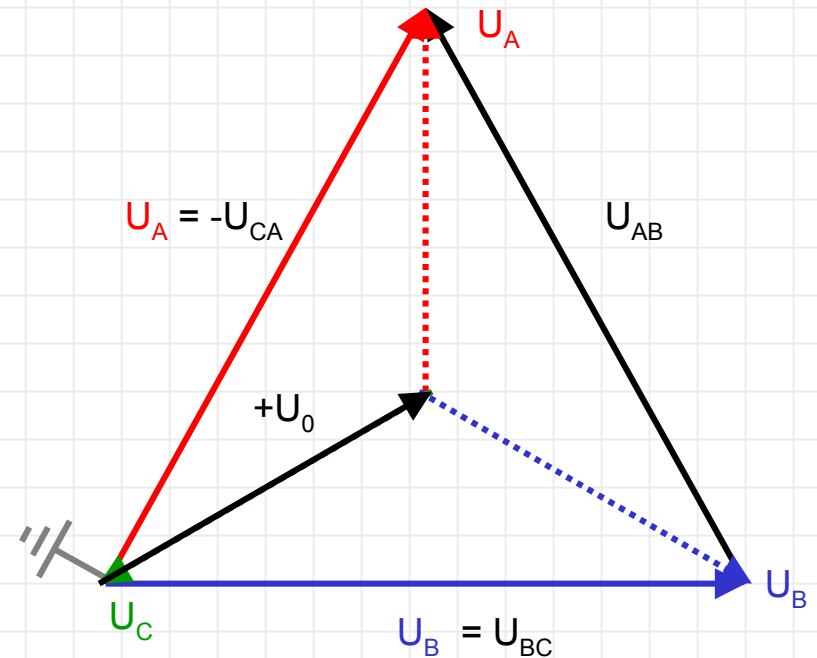


Voltage phasors after the fault


- Faulty phase voltage  $U_C = 0$
- Healthy phase voltages equal the line voltages
- Note the direction of the voltage  $+U_0$
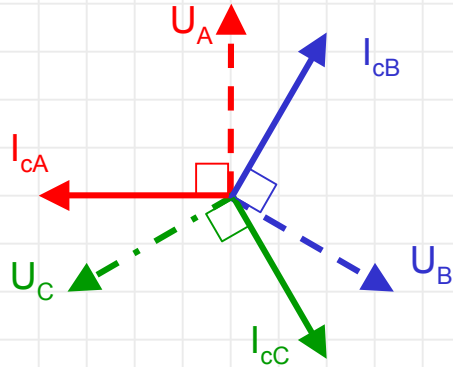
# Single phase to earth fault in unearthed network

Single-phase to earth fault in phase C - What happens to currents ?



Charge current phasors before the fault

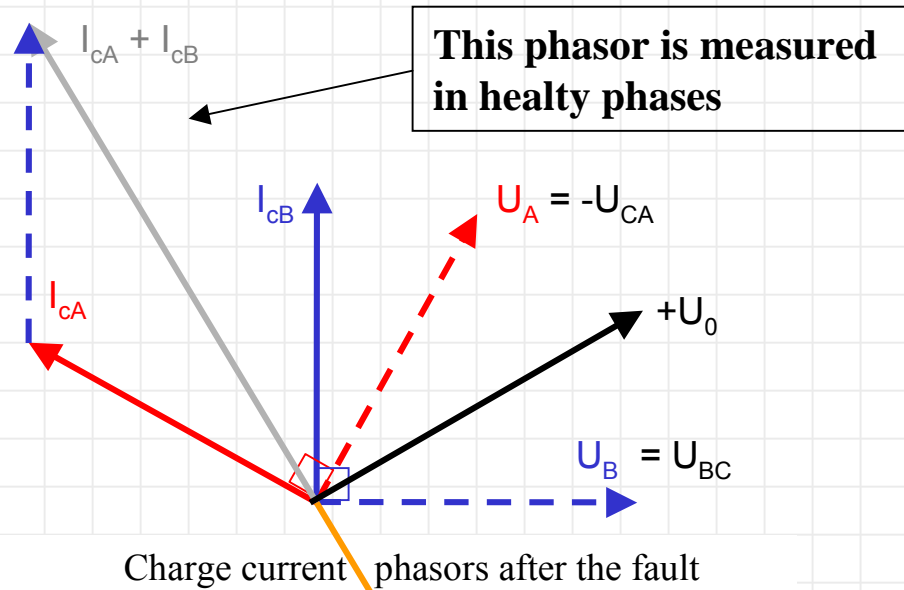

Charge current phasors after the fault


- Charging current leads corresponding phase voltage by  $90^\circ$
- The direction of the earth fault current is opposite to that of the charging current in healthy phases:  $I_{ef}$  vs.  $(I_{cA} + I_{cB}) = 180^\circ$  (see figure in slide 2 !)

**This phasor is the earth fault current**

# Single phase to earth fault in unearthed network
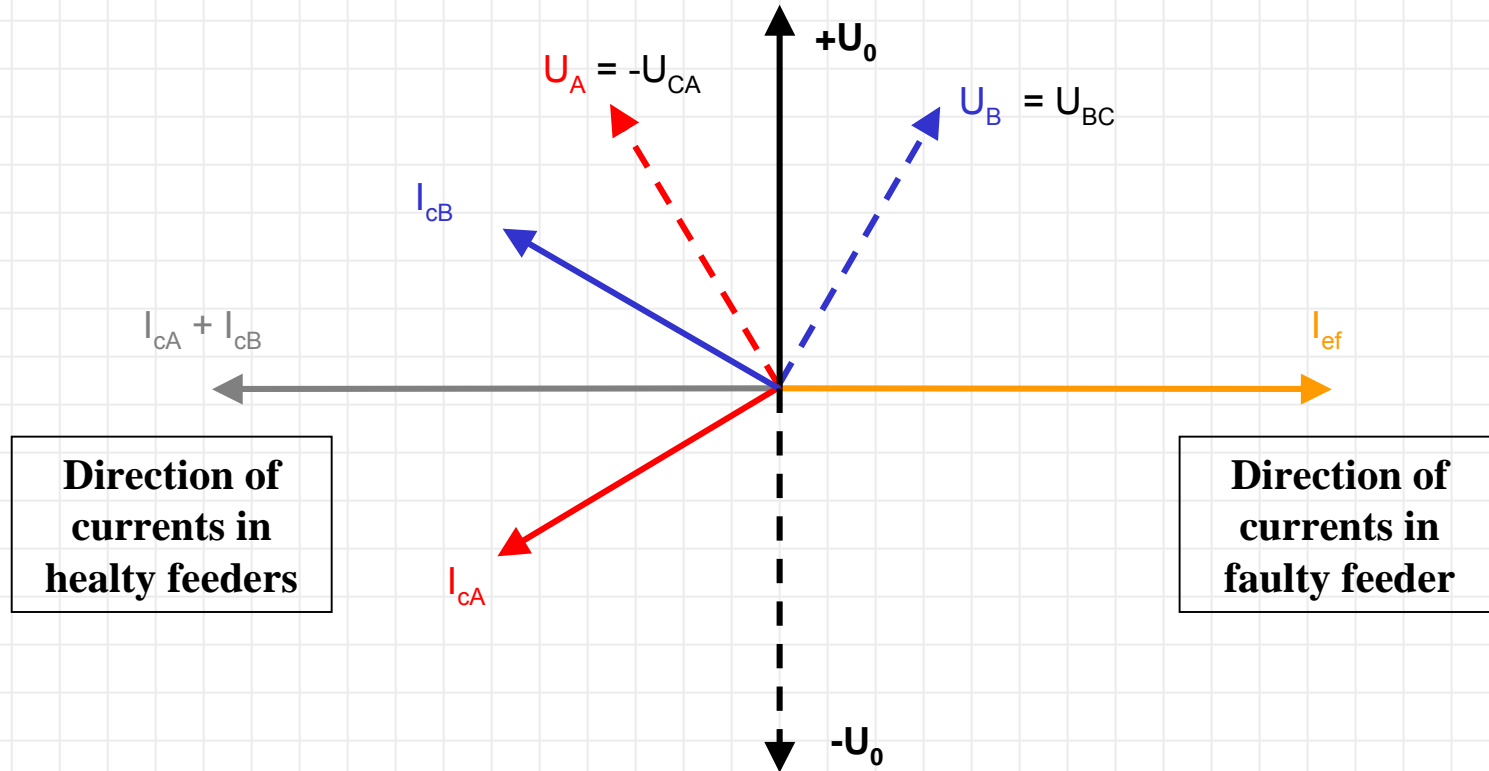
## Single-phase to earth fault in phase C - What happens to currents ?

- By turning the  $+U_0$ -phasor in order to have it pointing upwards, the previous figure can be drawn as:




- NOTE that in REF the characteristics for directional earth fault protection are drawn using  $-U_0$

# Single phase to earth fault in unearthed network
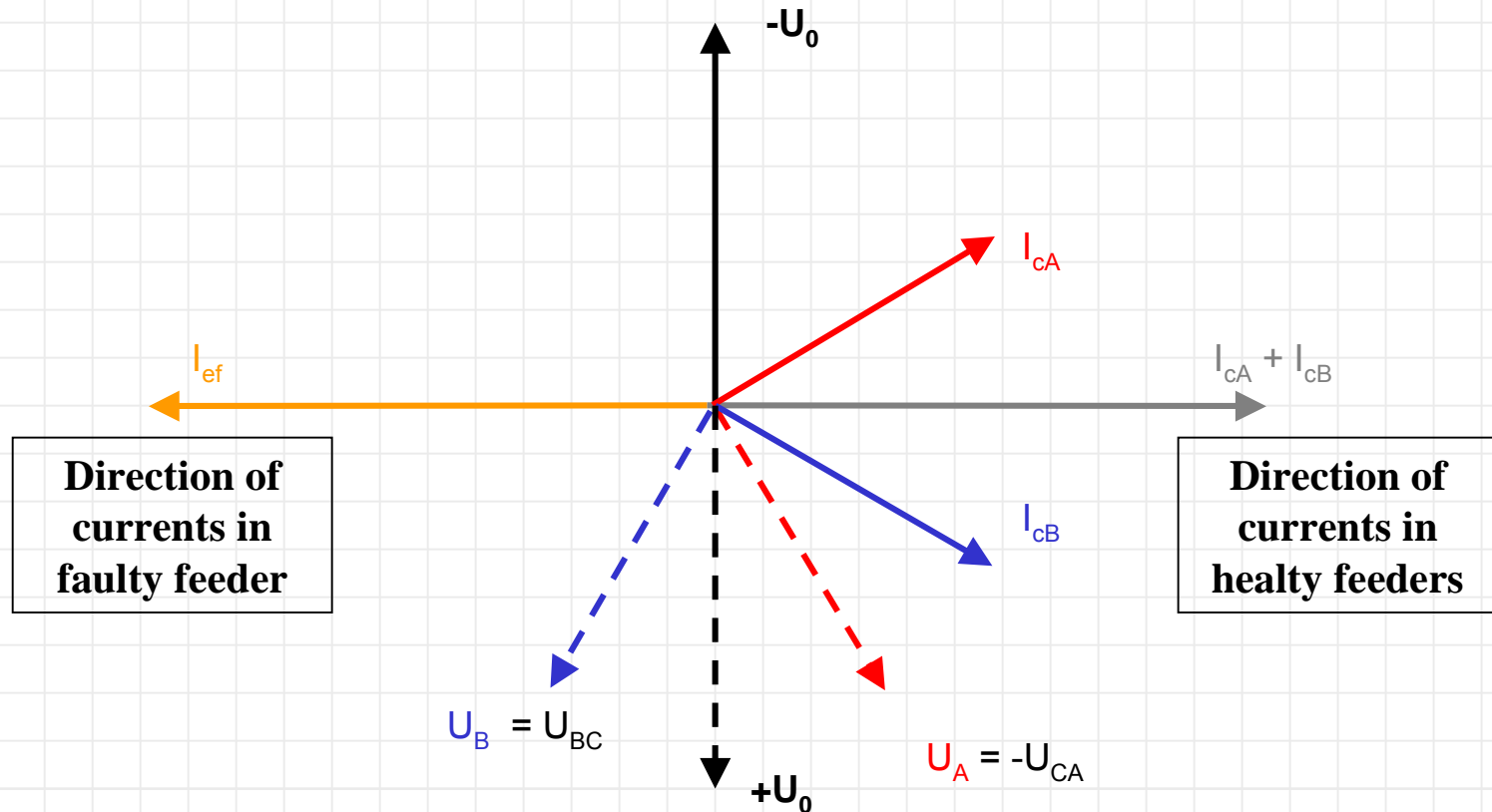
## Single-phase to earth fault in phase C - What happens to currents ?

- By turning the phasors so that  **$-U_0$ -phasor** is pointing upwards, the previous figure can be drawn as:




- In REF the characteristics for directional earth fault protection are drawn using  $-U_0$

# Earth fault in unearthed network


## Assumptions:

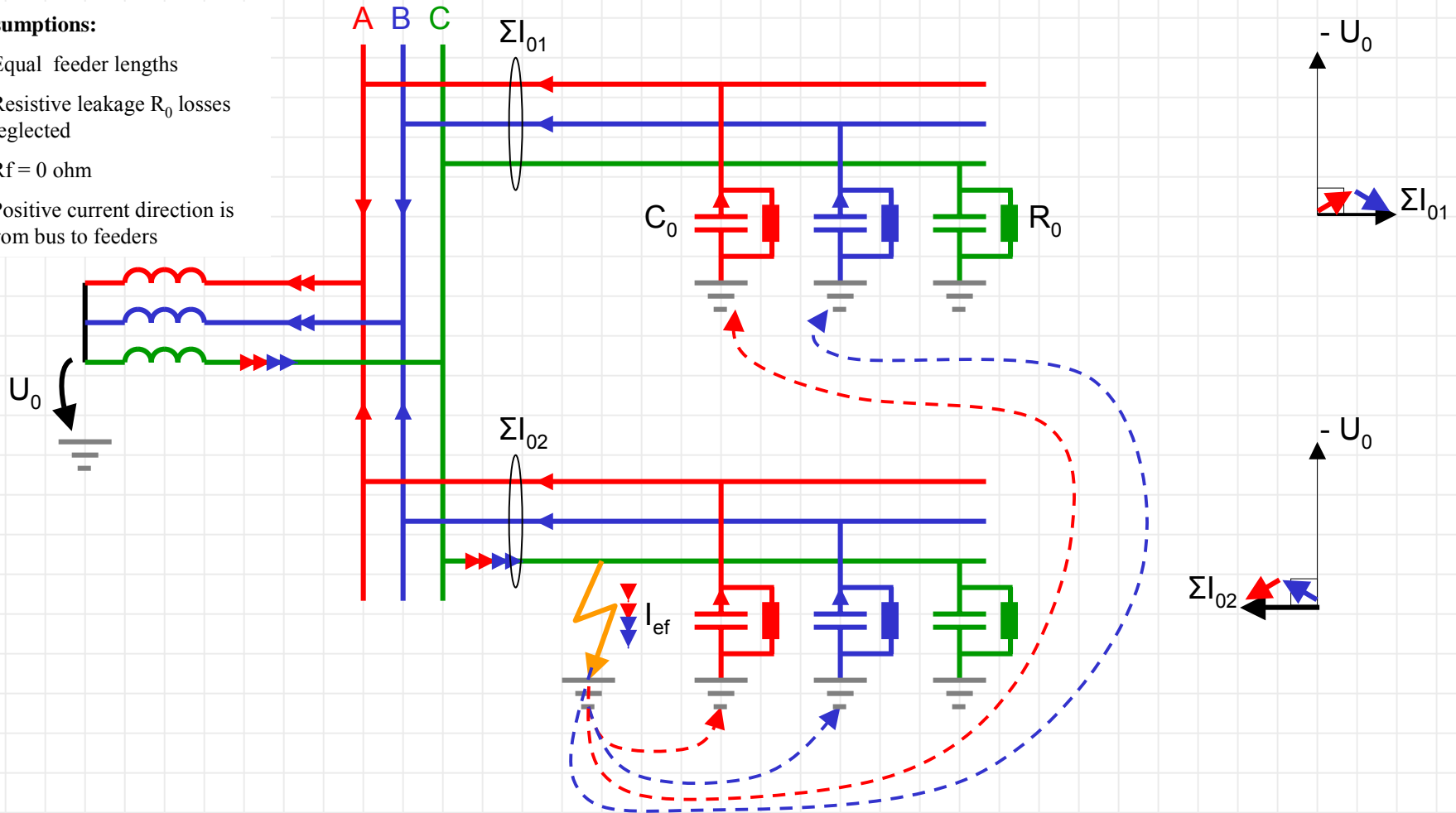1. Equal feeder lengths
2. Resistive leakage  $R_0$  losses neglected
3.  $R_f = 0$  ohm
4. Positive current direction is from bus to feeders



- $\Sigma I_{02} \neq I_{ef}$
- $I_0$  measurement in healthy feeder ( $\Sigma I_{01}$ ) includes only charging currents (healthy phases) of that feeder
- $I_0$  measurement in faulty feeder ( $\Sigma I_{02}$ ) includes charging currents of the galvanically connected background network, but not the charging currents of its own (these flow in both directions through the measurement point and cancel each other)
- Directional EF-protection is based on the angle of measured  $I_0$  versus  $U_0$  ( $-U_0$  in REF)

## Equivalent circuit

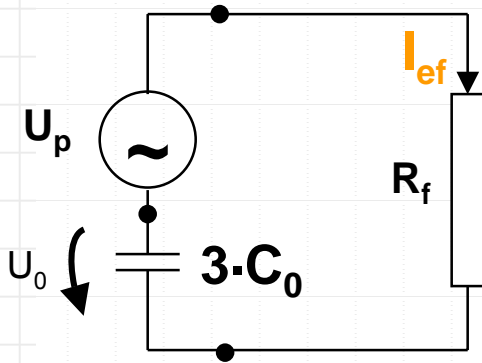

$$U_0 = \frac{I_{ef}}{3 \cdot \omega \cdot C_0} = \frac{U_p}{\sqrt{1 + (3 \cdot \omega \cdot C_0 \cdot R_f)^2}}$$


- $U_0$  is the voltage drop which is created when  $I_{ef}$  flows through the phase-to-earth capacitances
- $R_f$  is **NOT** included in these!!! See equivalent circuit!!!



# Earth fault in 100% compensated network


## Assumptions:

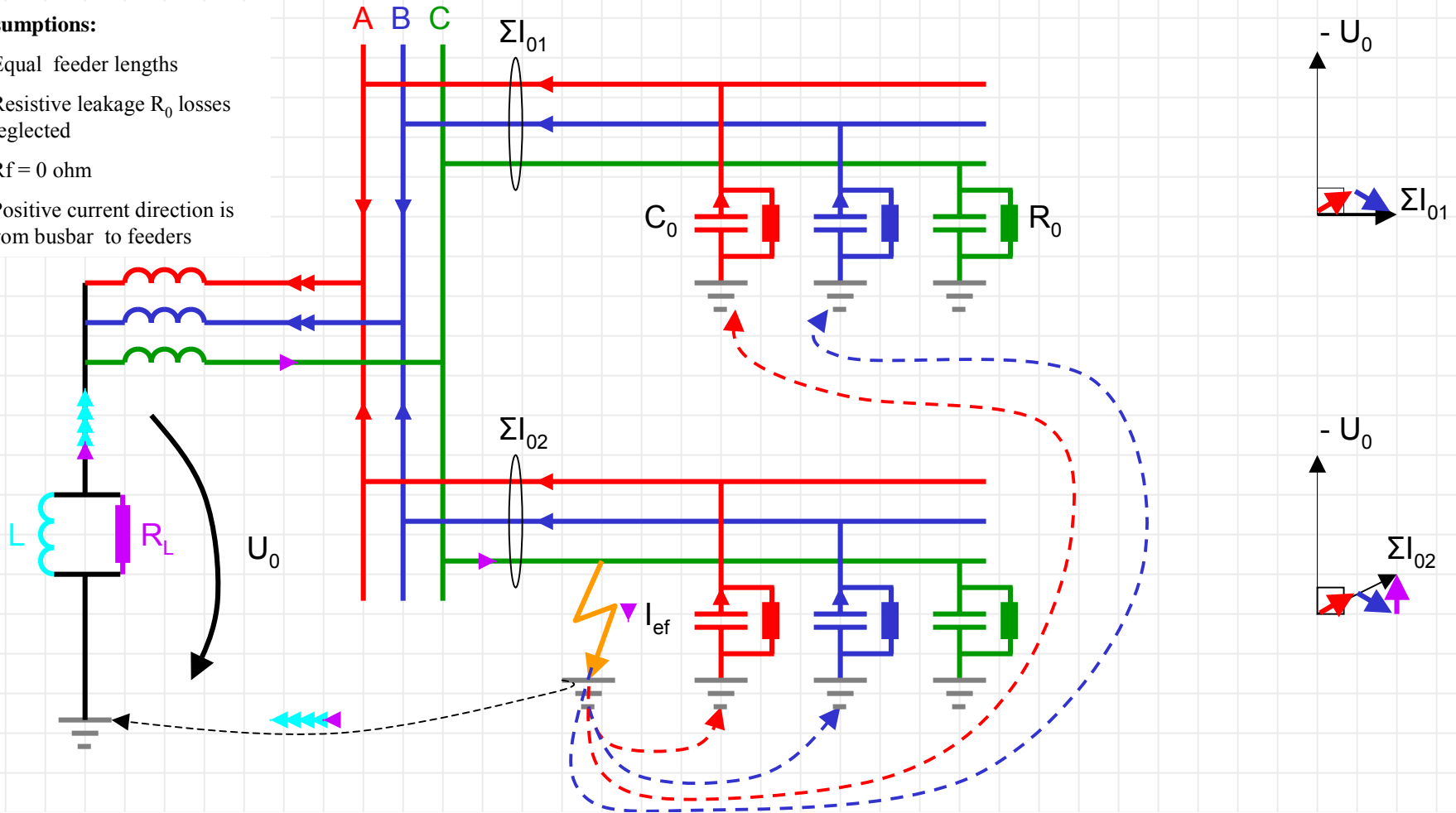1. Equal feeder lengths
2. Resistive leakage  $R_0$  losses neglected
3.  $R_f = 0$  ohm
4. Positive current direction is from busbar to feeders



- Earth-fault current is cancelled by feeding an equal inductive current with a compensation coil
- $I_0$  measurement in healthy feeder ( $\Sigma I_{01}$ ) includes only charging currents (healthy phases) of that feeder
- $I_0$  measurement in faulty feeder ( $\Sigma I_{02}$ ) includes now both the resistive current created by the additional resistor and its own charging currents
- Directional EF-protection is based on the angle of measured  $I_0$  versus  $U_0$  ( $-U_0$  in REF)

## Equivalent circuit

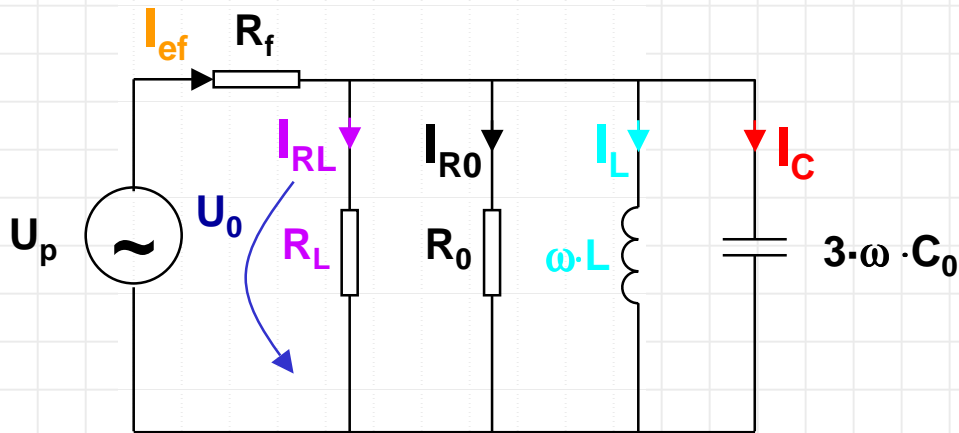


$$U_0 = \frac{I_{ef}}{\sqrt{\left(\frac{1}{R_0}\right)^2 + \left(3 \cdot \omega \cdot C_0 - \frac{1}{\omega \cdot L}\right)^2}}$$

- $U_0$  is the voltage drop which is created when  $I_{ef}$  flows through the impedance of the parallel connection of phase-to-earth capacitances, reactor  $L$ , additional resistor  $R_L$  and leakage resistance  $R_0$  of the lines
- $R_f$  is **NOT** included in these!!! See equivalent circuit!!!

# Earth fault in 50% under-compensated network

## Assumptions:

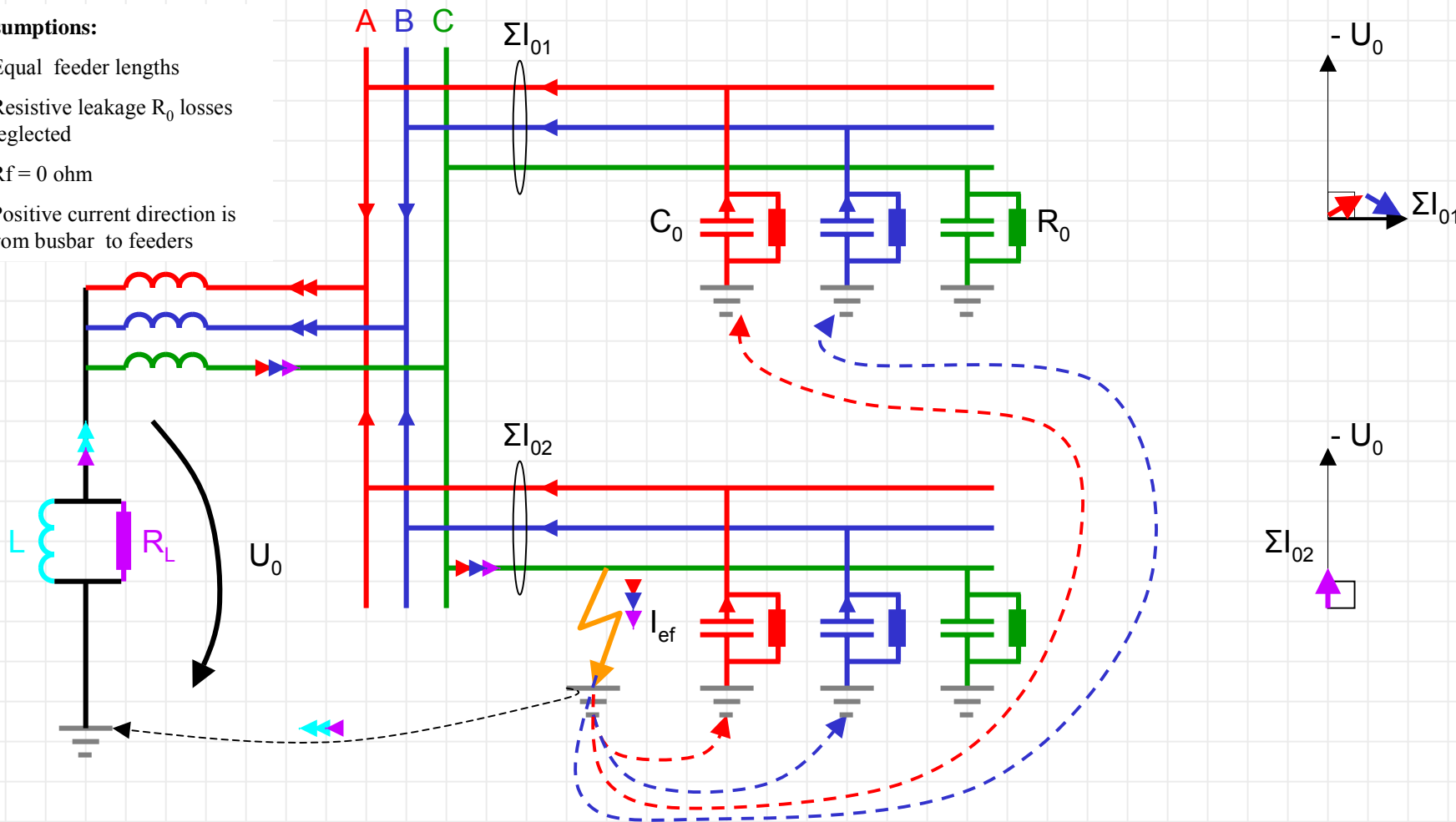1. Equal feeder lengths
2. Resistive leakage  $R_0$  losses neglected
3.  $R_f = 0$  ohm
4. Positive current direction is from busbar to feeders




- 50% of the earth-fault current is cancelled by feeding an inductive current with a compensation coil
- $I_0$  measurement in healthy feeder ( $\Sigma I_{01}$ ) includes only charging currents (healthy phases) of that feeder
- $I_0$  measurement in faulty feeder ( $\Sigma I_{02}$ ) includes now only the resistive current created by the additional resistor (background network's and feeders charging current flow in opposite directions in the measurement point and cancel each other)
- Directional EF-protection is based on the angle of measured  $I_0$  versus  $U_0$  ( $-U_0$  in REF)

# Earth fault in 150% over-compensated network

**Assumptions:**

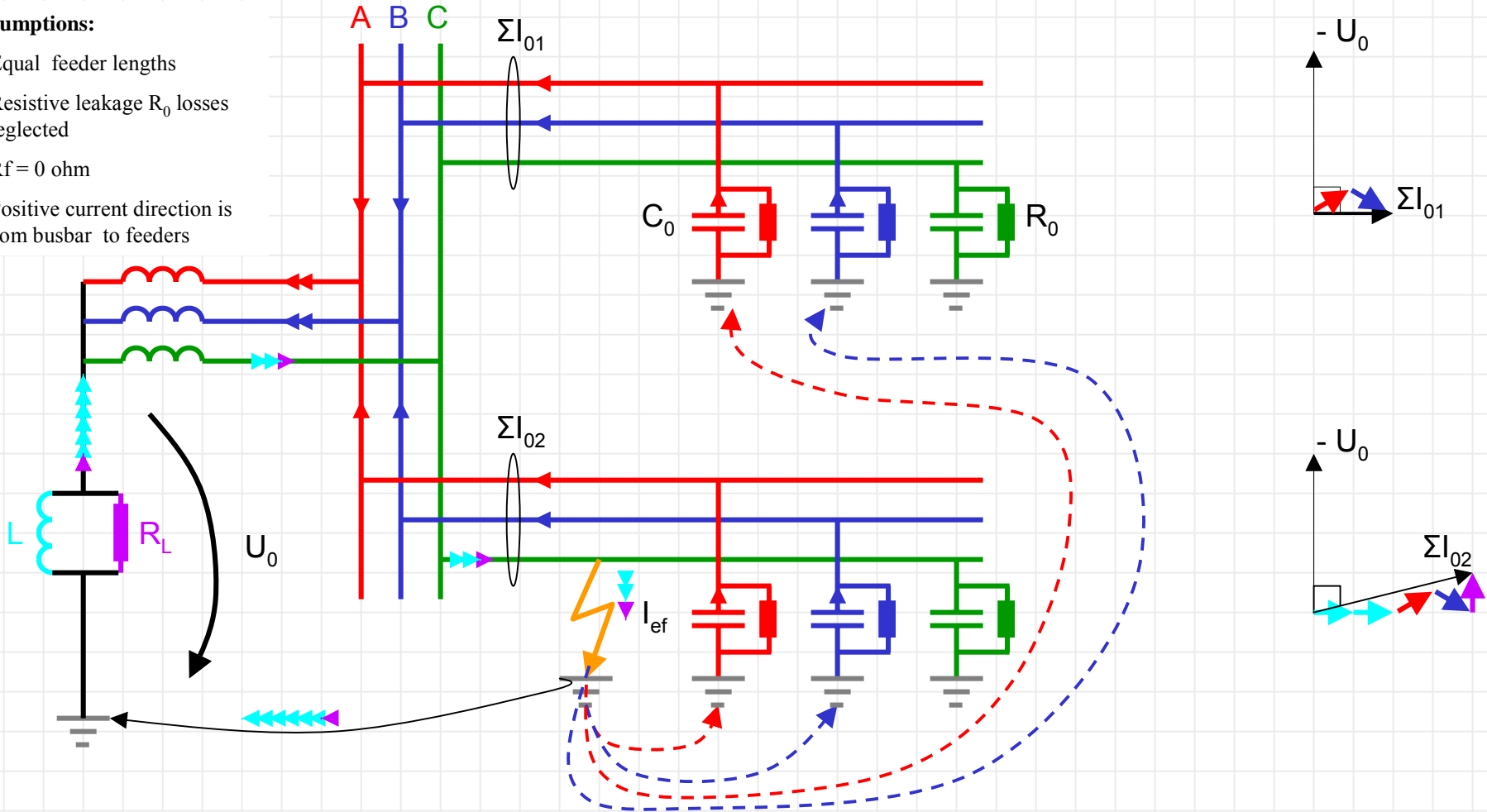1. Equal feeder lengths
2. Resistive leakage  $R_0$  losses neglected
3.  $R_f = 0$  ohm
4. Positive current direction is from busbar to feeders




- 150% of the earth-fault current is cancelled by feeding an inductive current with a compensation coil
- $I_0$  measurement in healthy feeder ( $\Sigma I_{01}$ ) includes only charging currents (healthy phases) of that feeder
- $I_0$  measurement in faulty feeder ( $\Sigma I_{02}$ ) includes now both the resistive current created by the additional resistor, its own charging currents and the overrest of the inductive current
- Directional EF-protection is based on the angle of measured  $I_0$  versus  $U_0$  ( $-U_0$  in REF)

# Earth fault in high resistance earthed network


## Assumptions:

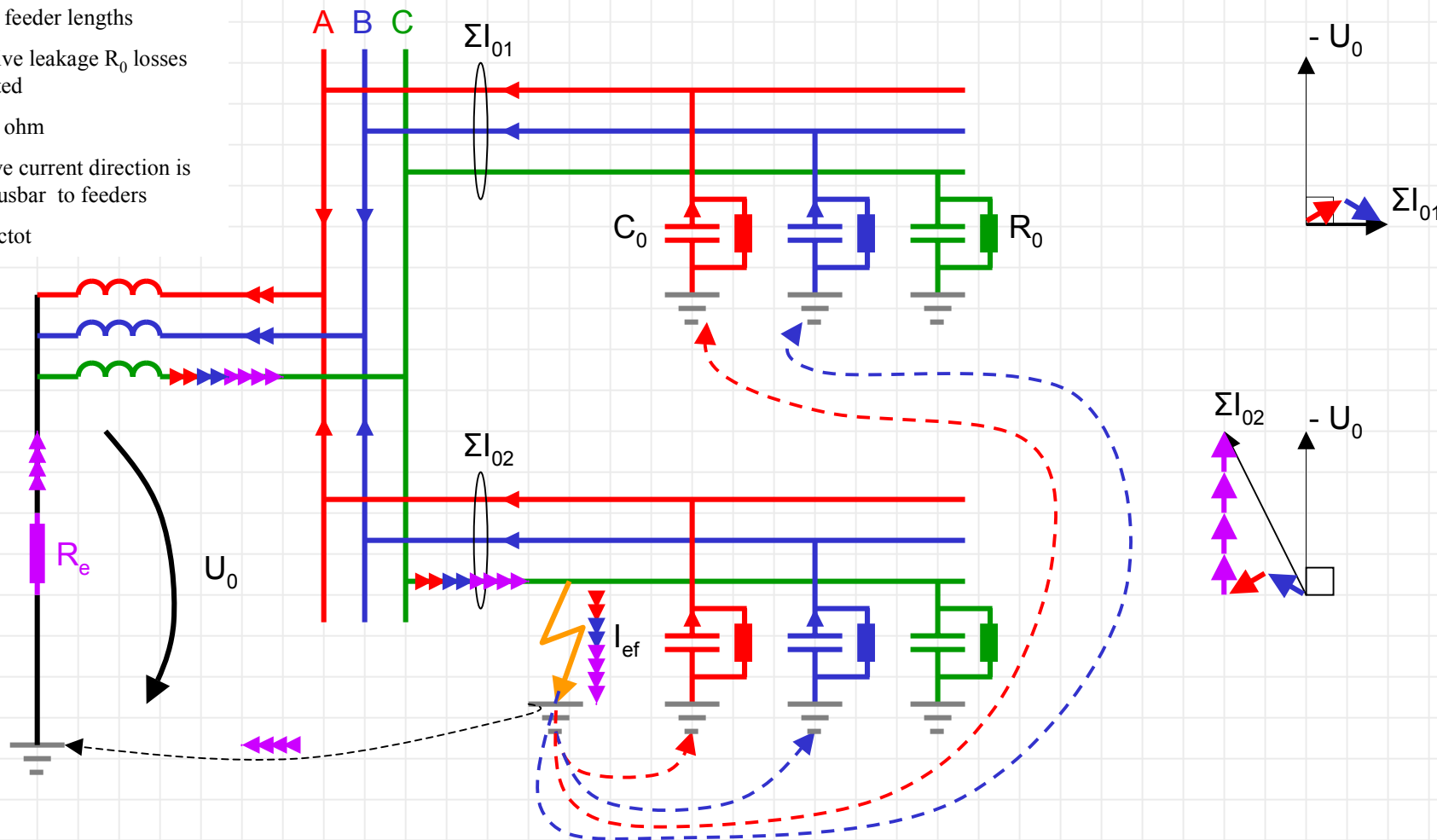1. Equal feeder lengths
2. Resistive leakage  $R_0$  losses neglected
3.  $R_f = 0$  ohm
4. Positive current direction is from busbar to feeders
5.  $I_{Re} = I_{ctot}$



- Earth-fault current includes a resistive part defined by the size of  $R_e (\leq 1/(3 \cdot \omega \cdot C_{0tot}))$
- $I_0$  measurement in healthy feeder ( $\Sigma I_{01}$ ) includes only charging currents (healthy phases) of that feeder
- $I_0$  measurement in faulty feeder ( $\Sigma I_{02}$ ) includes now both the resistive current created by the earthing resistor and capacitive charging current of the galvanically connected background network
- Directional EF-protection is based on angle of measured  $I_0$  versus  $U_0$  ( $-U_0$  in REF)

## Equivalent circuit

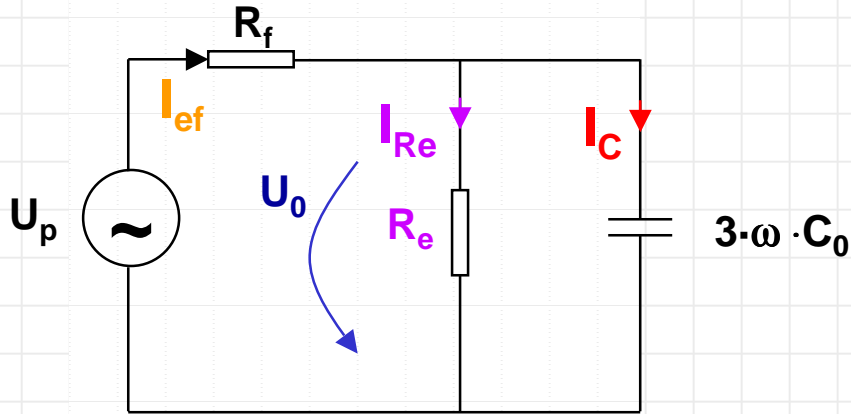

$$U_0 = \frac{I_{ef}}{\sqrt{\left(\frac{1}{R_e}\right)^2 + (3 \cdot \omega \cdot C_0)^2}}$$

- $U_0$  is the voltage drop which is created when  $I_{ef}$  flows through the impedance of the parallel connection of phase-to-earth capacitances and earthing resistor  $R_e$
- $R_f$  is **NOT** included in these!!! See equivalent circuit!!!